

How 2 blink LEDs


Joshua Fleming





About me

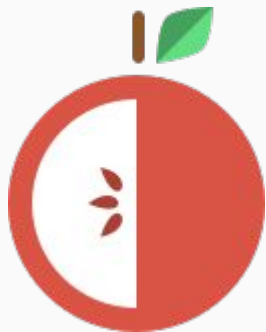- Computer Engineer, '19
- Cybersecurity Club - Secretary
- STICs Facilitator - CMSC389R
- Bitcamp Organizer - Hardware




Follow Along

- Code and slides available at <https://github.com/jsfleming/bitcamp-led-workshop>



Electronics Fundamentals

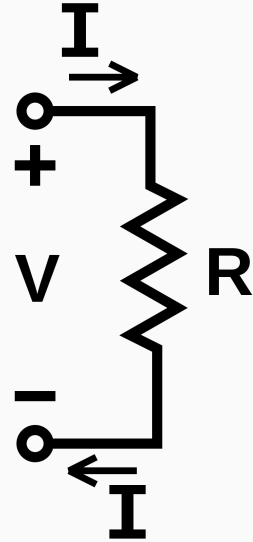- Voltage: “force” to drive current through components
- Current: flow of charge through components
- Resistance: “force” against current
- $V = I \times R$



Types of components

- Resistors: devices that add resistance in a circuit
 - Necessary to prevent too much current
 - Too much current = smoking, fire, explosions, etc
- Capacitors: devices that can store charge temporarily
 - As long as a voltage difference is applied, capacitors will fill with charge
 - Discharge as voltage difference decreases
- Diodes: allow current to flow only one way
 - LEDs are diodes that light up!

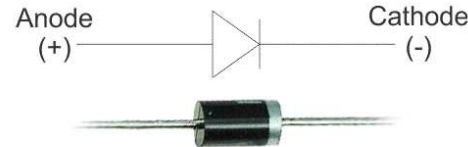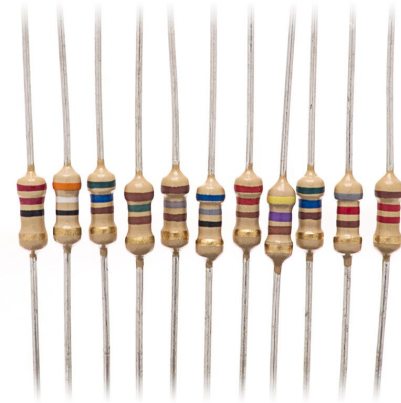


Types of components

- Sensors: detect physical properties and convert to something usable in a circuit
 - Photoresistor: resistor that decreases as light increases
 - Thermister: resistor that decreases as heat increases
 - Proximity sensor: detects proximity to device and represents as voltage, resistance, number, etc (dependent on sensor)




Types of components

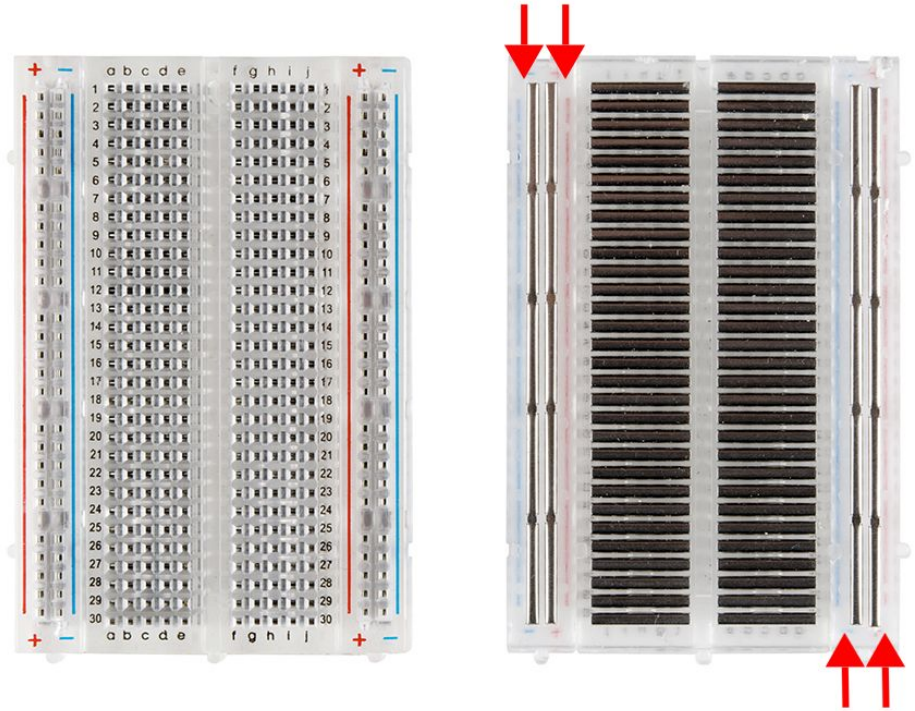- Breadboard
 - Connect stuff together
 - Power rails vertical
 - Main board rails horizontal



Turning on an LED

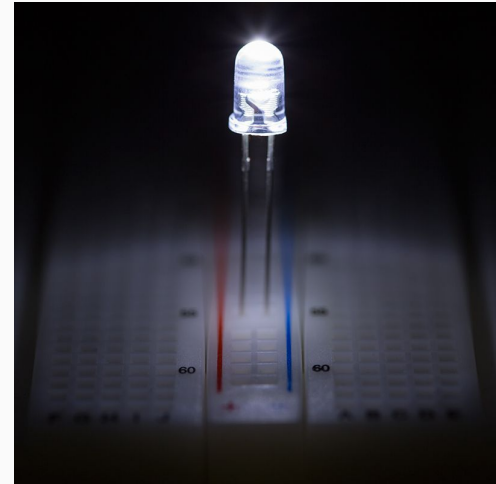- Voltage difference across LED will make it glow
- CAUTION: diodes don't stop current from flowing
 - Put a resistor in between LED and voltage source
 - Can actually explode an LED w/ too much current




Onto the circuits!

Basic circuit

- We'll be using the Arduino for our power source (for now)
- Plug in the Arduino to your computer
- Share with others who have a kit!


Basic circuit

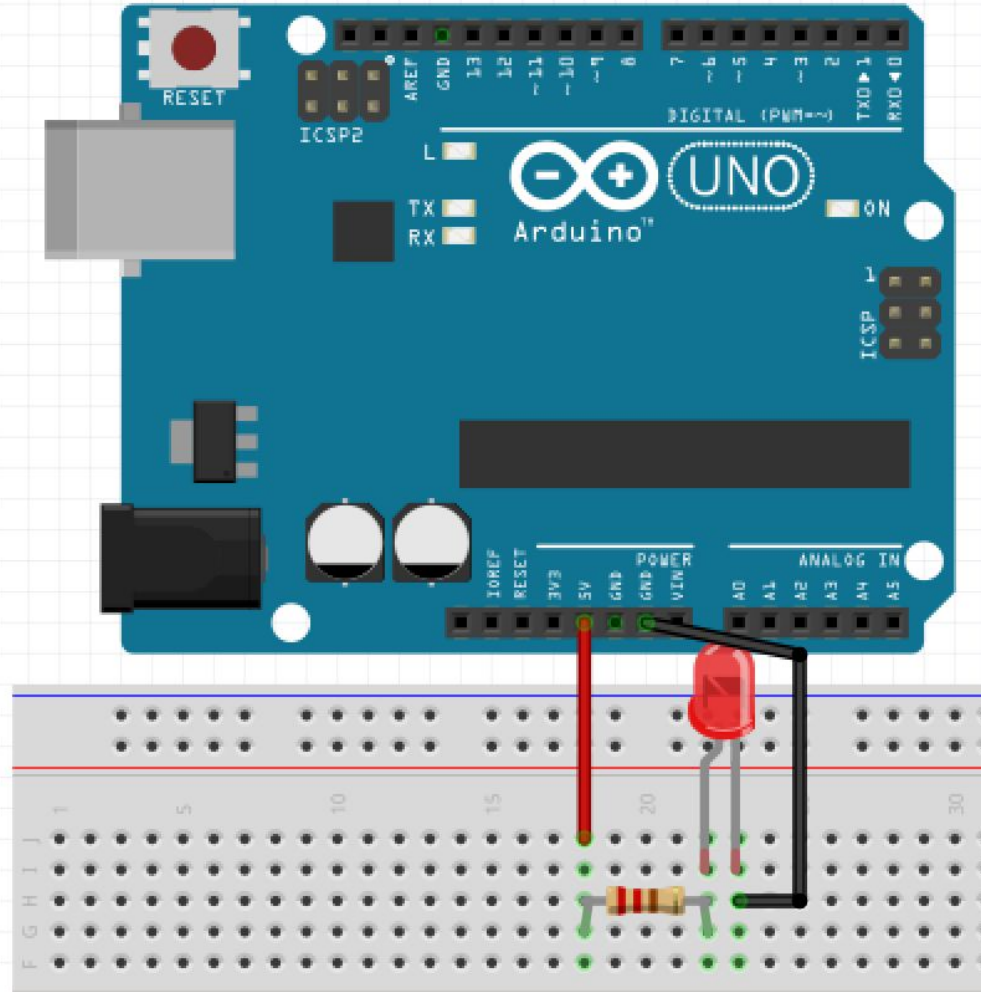- LED
 - Longer leg = higher voltage
 - Shorter leg = lower voltage
- Resistor




Fancy circuit

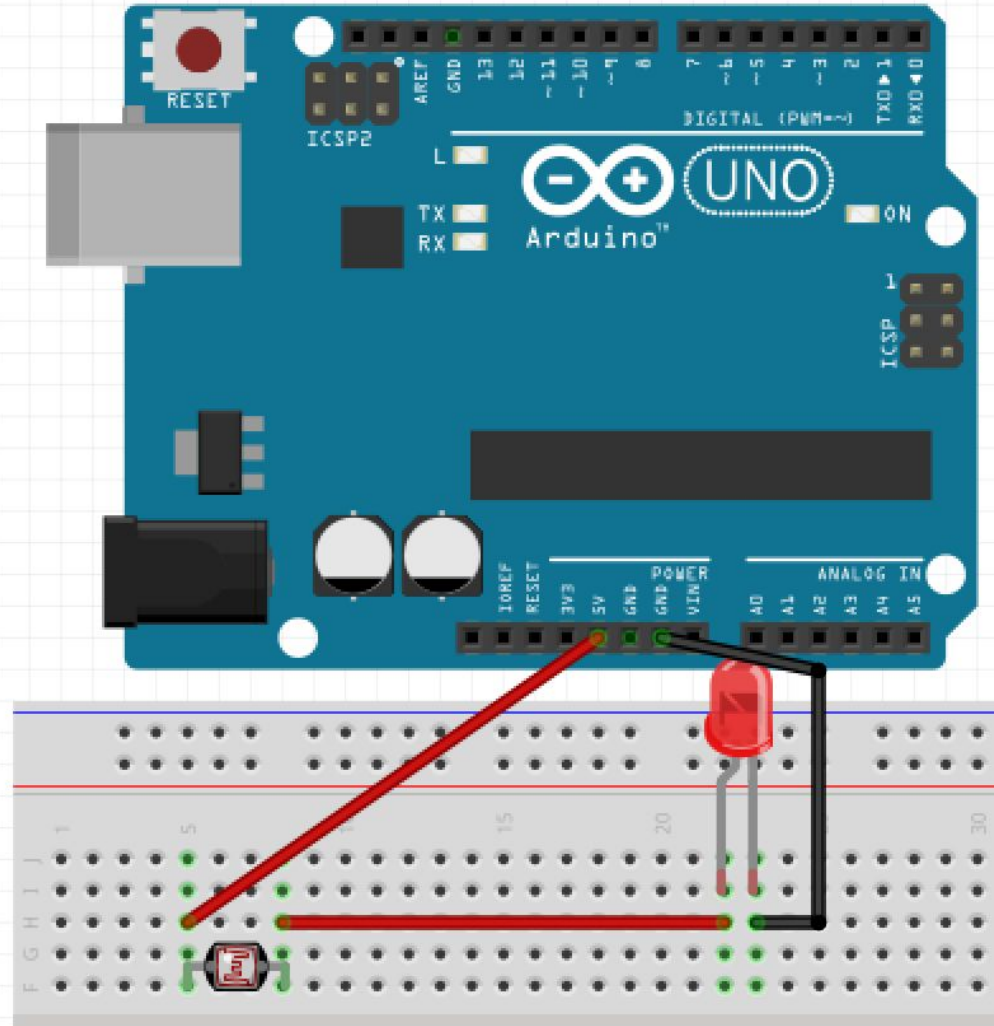- LED
 - Longer leg = higher voltage
 - Shorter leg = lower voltage
- Photoresistor
 - LED strength changes with light
 - Shine your phone's light against the photoresistor to see the LED brightness change!
 - Keep this a bit farther away from LED to see the changes



Button circuit

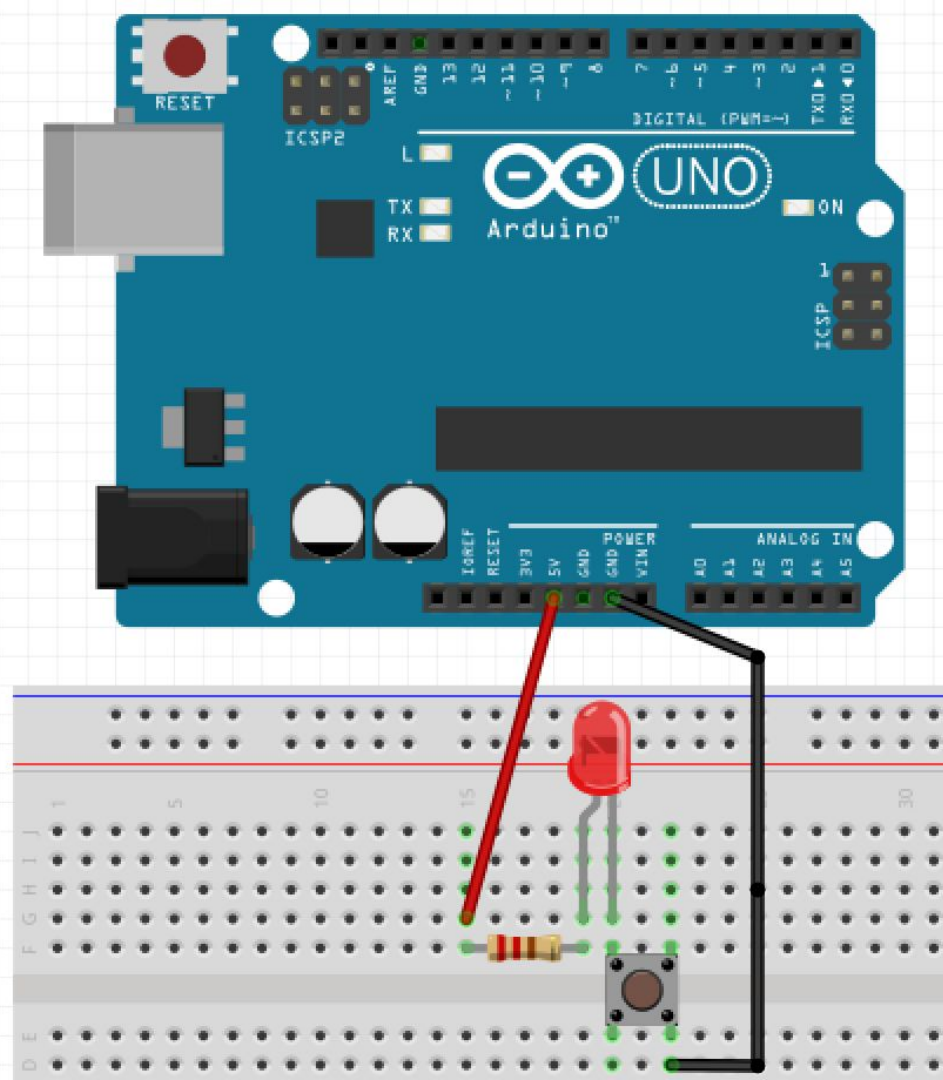- LED
 - Longer leg = higher voltage
 - Shorter leg = lower voltage
- Resistor
- Button
 - Terminals connected diagonally when button pressed
 - i.e. top left -> bottom right, etc



Controlling with Arduino!



Arduino Programming

- Uses a C-like language
- Basic, easy to pick up
- Lots of libraries to make writing code faster and easier

Arduino Fundamentals

- `void setup()`
 - This function runs once
 - Use to set variables to initial values
- `void loop()`
 - This function runs indefinitely
 - Program body will go here
- Declare variables outside of functions

```
#include "some_library.h"

int number;

void setup() {
    number = 0;
}

void loop() {
    number = number + 1;
}
```


Arduino Fundamentals

- `pinMode(PIN, MODE)`
 - Use to declare pins on Arduino to receive input or to send outputs
 - PIN is pin number
 - MODE is either INPUT or OUTPUT
- Digital pins: 0, 1, 2, 3, ... 13
 - Pins with ~ can use PWM
 - PWM is “fake” analog using digital pins -- can write values from 0 to 255
- Analog pins: A0, A1, ..., A5
 - Read values from 0 to 1023
 - Analog pins can ONLY be input

Arduino Fundamentals

- `digitalRead(PIN)` - returns HIGH or LOW from pin PIN
- `digitalWrite(PIN, HIGH or LOW)` - writes HIGH or LOW to pin PIN
- `analogRead(PIN)` - returns value from 0 to 255
- `analogWrite(PIN, VALUE)` - writes a value VALUE from 0 to 255 to pin PIN

- `Serial.begin(BAUD_RATE)` - sets up printing on Serial console
 - Tools > Serial Monitor
- `Serial.print(STUFF)` - prints STUFF to Serial console
- `delay(MILLISECONDS)` - pause code execution for some MILLISECONDS
 - 1s = 1000ms

Arduino Fundamentals

- `digitalRead(PIN)` - returns HIGH or LOW from pin PIN
- `digitalWrite(PIN, HIGH or LOW)` - writes HIGH or LOW to pin PIN
- `analogRead(PIN)` - returns value from 0 to 255
- `analogWrite(PIN, VALUE)` - writes a value VALUE from 0 to 255 to pin PIN
- `Serial.begin(BAUD_RATE)` - sets up printing on Serial port
 - Tools > Serial Monitor
- `Serial.print(STUFF)` - prints STUFF to Serial console

```
int digitalPin = 2;
int analogPin = A3;
int pwmPin = 11;

int val;
int num;

void setup() {
  pinMode(digitalPin, INPUT);
  pinMode(analogPin, INPUT);
  pinMode(pwmPin, OUTPUT);
  Serial.begin(9600);
}

void loop() {
  val = digitalRead(digitalPin);
  num = analogRead(analogPin);
  digitalWrite(pwmPin, HIGH);
  delay(100);
  digitalWrite(pwmPin, LOW);
  analogWrite(pwmPin, 135);

  Serial.print("Digital Value:\n");
  Serial.print(val);
  Serial.print("Analog Number:\n");
  Serial.println(num);
}
```


Circuits with Arduino!

Essence of Arduino Projects

- Figure out what you want to do
- Determine what parts you need
 - Which parts generate something? (motors, speakers, lights, etc)
 - Which parts detect something? (sensors, buttons, switches, scanners, etc)
- Use Arduino to control external components
 - digital/analog write for outputs (motors, speakers, lights, etc)
 - digital/analog read for inputs (sensors, buttons, switches, scanners, etc)
- Write program to perform task
 - What does something
 - When to do something
 - How long to do something


Blinky Circuit

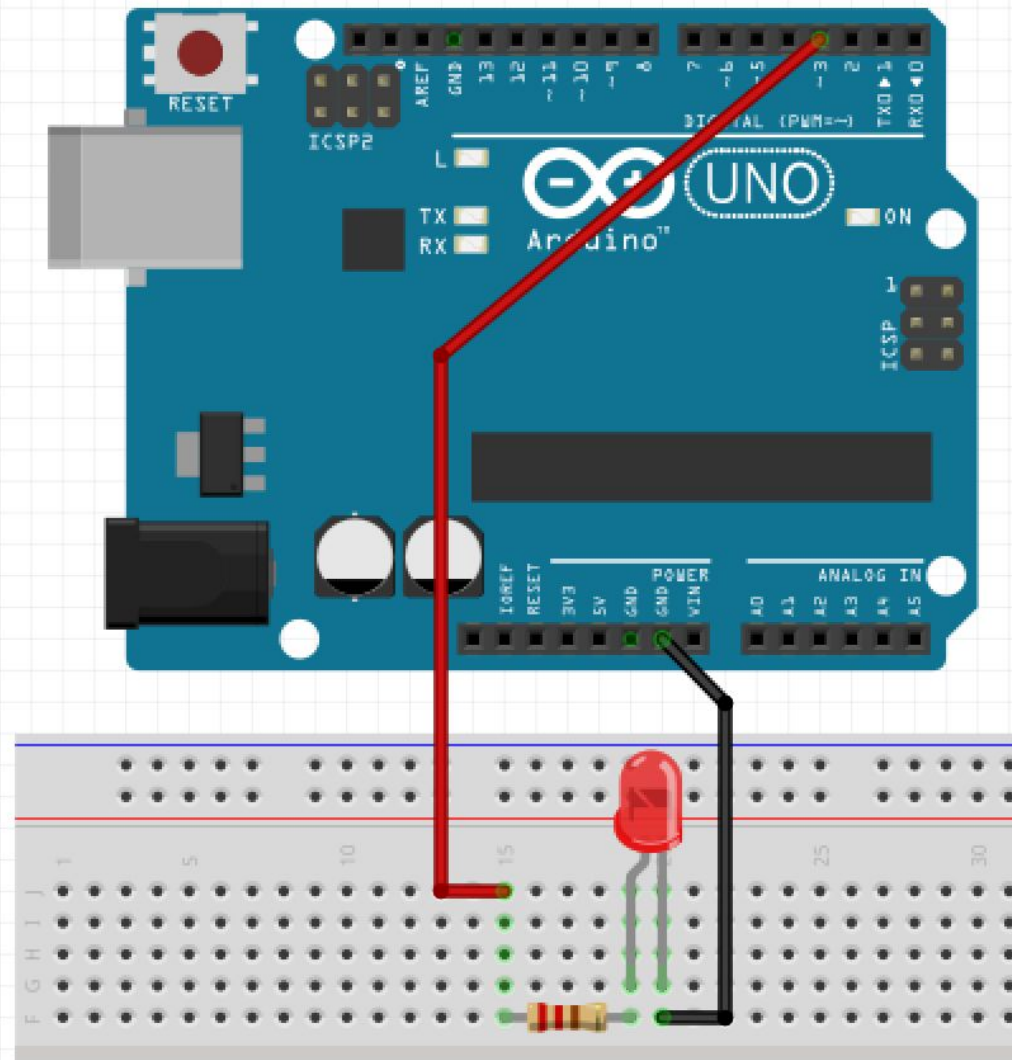- Arduino
- LED
 - Longer leg = higher voltage
 - Shorter leg = lower voltage
- Resistor
- Controlled from pin 3
 - `digitalWrite`



Fancy Blinky Circuit

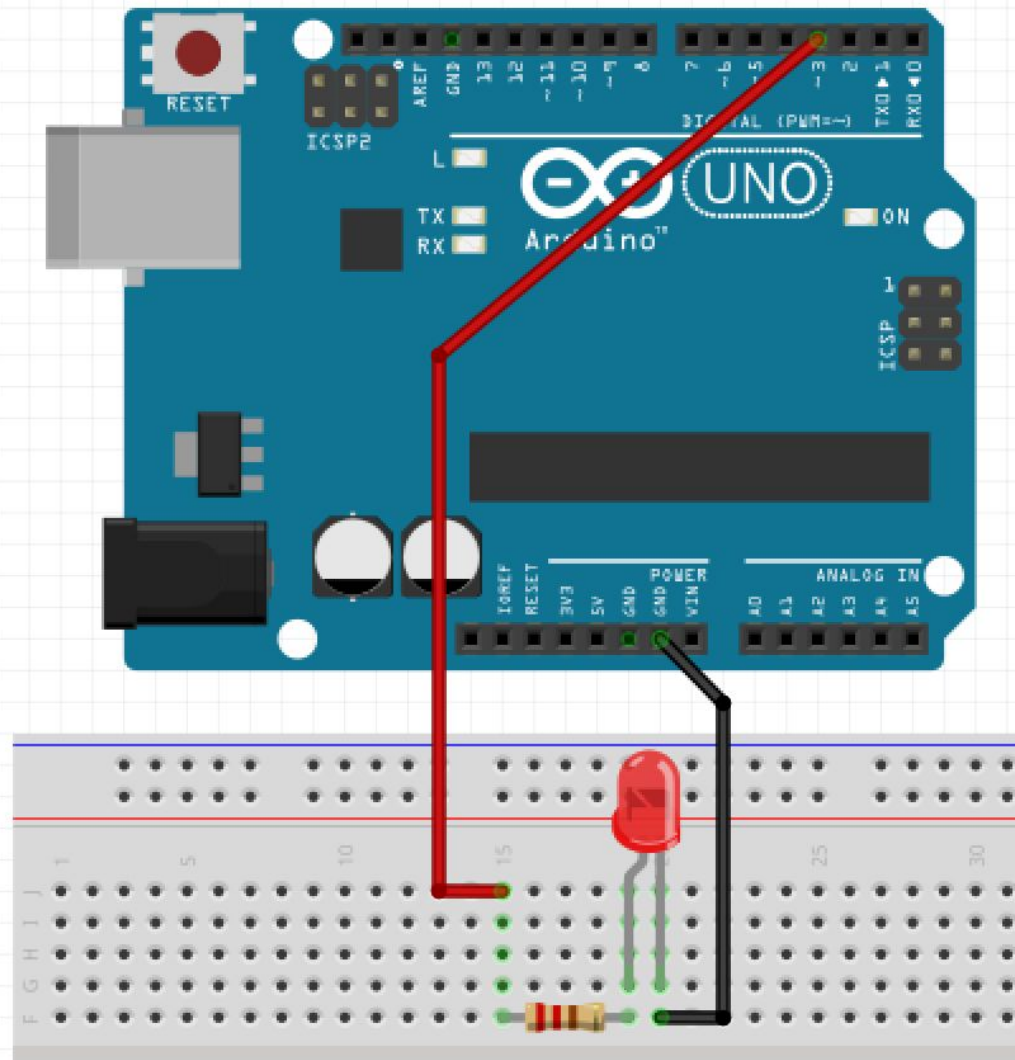- Arduino
- LED
 - Longer leg = higher voltage
 - Shorter leg = lower voltage
- Resistor
- Controlled from pin 3
 - `analogWrite`



Proximity Blinky Circuit

- Arduino
- LED - pin 3
 - Longer leg = higher voltage
 - Shorter leg = lower voltage
- Resistor
- Distance Sensor
 - Pin 9 -> TRIG
 - Pin 10 -> ECHO
 - 5V -> VCC
 - GND -> GND

